



ECB2181 – ELECTRONICS FOR MECHANICAL SYSTEMS

Assignment Part 1

Question numbers are given in the table:

RRN End with	Question No				
0	3	7	10	2	6
1	5	10	4	6	9
2	3	2	9	7	5
3	1	8	3	5	6
4	2	1	10	9	3
5	7	3	8	10	6
6	7	8	9	3	4
7	5	2	3	10	9
8	8	7	3	9	6
9	5	8	6	9	10

Questions:

1	Decimal	Binary	Octal	Hexadecimal
	$(34.6)_{10}$	$(1010110)_2$?	?
	$(446.25)_{10}$?	?	$(1BE.4)_{16}$
	?	$(1010111.011)_2$	$(127.3)_8$?

Show each conversion with proof

2	Decimal	Binary	Octal	Hexadecimal
	?	?	$(657)_8$	$(1AF)_{16}$
	?	$(11100101)_2$	$(345)_8$?
	$(67)_{10}$?	?	$(43)_{16}$

Show each conversion with proof

- 3 Perform 1's complement subtraction for the following
 - $(12)_{10} - (15)_{10}$
 - $(25)_8 - (32)_8$
 - $(1100)_2 - (1001)_2$
 - $(31F)_H - (12A)_H$
- 4 Perform 2's complement subtraction for the following
 - $(356)_{10} - (234)_{10}$
 - $(1234)_8 - (2313)_8$
 - $(10011)_2 - (10101)_2$
 - $(DEF)_H - (ABC)_H$
- 5 Draw all the logical gates with their expression and truth table



ECB2181 – ELECTRONICS FOR MECHANICAL SYSTEMS

- 6 Prove $x.x = x$ and $x+1 = 1$ using postulates
- 7 Draw logical diagram for the following functions:
 $F1 = XYZ'$
 $F2 = X+Y'Z$
 $F3 = X'Y'Z'+X'YZ+XY'$
 $F4 = XY'+X'Z$
- 8 Demonstrate by means of truth table the validity of the following identities:
 - (i) $(xyz)' = x'+y'+z'$
 - (ii) $x+yz = (x+y)(x+z)$
 - (iii) $xy+x'z+yz = xy+x'z$
- 9 Given the following Boolean function
 $F = xy'z + x'y'z + w'xy + wx'y + wxy$
 - a. Obtain the truth table of the function
 - b. Draw the logic diagram using the original Boolean expression
 - c. Simplify the function to minimum number of literals using Boolean algebra.
 - d. Obtain the truth table of the function from the simplified expression and show that it is the same as the one in part (a)
- 10 Simplify the following expression using K map
 $F(x,y,z) = \Sigma(2,3,4,5)$
 $F(x,y,z) = \Sigma(0,2,4,5,6)$
 $F = A'C + A'B + AB'C + BC$