

# Digital System Design

## Lecture 12

### Combinational Logic Design

### Binary Adder-Subtractor

#### Objectives:

1. Half Adder.
2. Full Adder.
3. Binary Adder.
4. Binary Subtractor.
5. Binary Adder-Subtractor.

#### 1. Half Adder

**Half Adder:** is a combinational circuit that performs the addition of two bits, this circuit needs two binary inputs and two binary outputs.

Inputs		Outputs	
X	Y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0


**Truth table**

The simplified Boolean function from the truth table:


$$\left. \begin{array}{l} S = \bar{X}Y + X\bar{Y} \\ C = XY \end{array} \right\} \text{ (Using sum of product form)}$$

Where **S** is the sum and **C** is the carry.
 
$$\left. \begin{array}{l} S = X \oplus Y \\ C = XY \end{array} \right\} \text{ (Using XOR and AND Gates)}$$



 Implementation of Half Adder using equation (1)



Implementation of Half Adder using equation (2)

- The implementation of half adder using **exclusive-OR** and an **AND** gates is used to show that two half adders can be used to construct a full adder.
- The inputs to the **XOR** gate are also the inputs to the **AND** gate.

## 2. Full Adder

**Full Adder** is a combinational circuit that performs the addition of three bits (two significant bits and previous carry).

- It consists of **three inputs and two outputs**, two inputs are the bits to be added, the third input represents the carry form the previous position.
- The full adder is usually a component in a cascade of adders, which add 8, 16, etc, binary numbers.

Inputs			Outputs	
X	Y	C <sub>in</sub>	S	C <sub>out</sub>
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

*Truth table for the full adder*

- The **S** output is equal to **1** when only one input is equal to **1** or when all three inputs are equal to **1**.
- The **C<sub>out</sub>** output has a carry **1** if two or three inputs are equal to **1**.
- The Karnaugh maps and the simplified expression are shown in the following figures:

X \ YC <sub>in</sub>	00	01	11	10
0	0	1	0	1
1	1	0	1	0


$$S = \overline{X}\overline{Y}C_{in} + \overline{X}Y\overline{C_{in}} + X\overline{Y}\overline{C_{in}} + XYC_{in}$$

X \ YC <sub>in</sub>	00	01	11	10
0	0	0	1	0
1	0	1	1	1

$$C_{out} = XY + XC_{in} + YC_{in}$$

$$\left. \begin{cases} S = \overline{X}\overline{Y}C_{in} + \overline{X}Y\overline{C_{in}} + X\overline{Y}\overline{C_{in}} + XYC_{in} \\ C_{out} = XY + XC_{in} + YC_{in} \end{cases} \right\} \text{1 (Sum of products)}$$

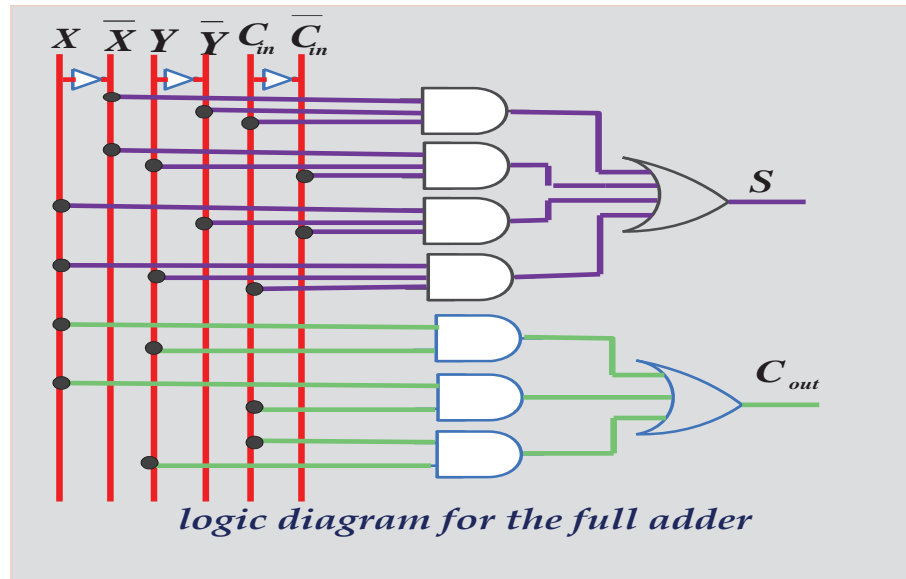- The *logic diagrams* for the full adder implemented in *sum-of-products* form are the following:



- It can also be implemented using *two half adders* and *one OR gate* (using **XOR** gates).

$$\left\{ \begin{array}{l} S = C_{in} \oplus (X \oplus Y) \\ C_{out} = C_{in} \cdot (X \oplus Y) + XY \end{array} \right\}$$


**Proof:**

**The sum:**

$$\begin{aligned} S &= \bar{X}\bar{Y}C_{in} + \bar{X}Y\bar{C}_{in} + X\bar{Y}\bar{C}_{in} + XYC_{in} \\ &= \bar{C}_{in}(\bar{X}Y + X\bar{Y}) + C_{in}(\bar{X}\bar{Y} + XY) \\ &= \bar{C}_{in}(\bar{X}Y + X\bar{Y}) + C_{in}(\overline{\bar{X}\bar{Y} + XY}) \\ S &= C_{in} \oplus (X \oplus Y) \end{aligned}$$

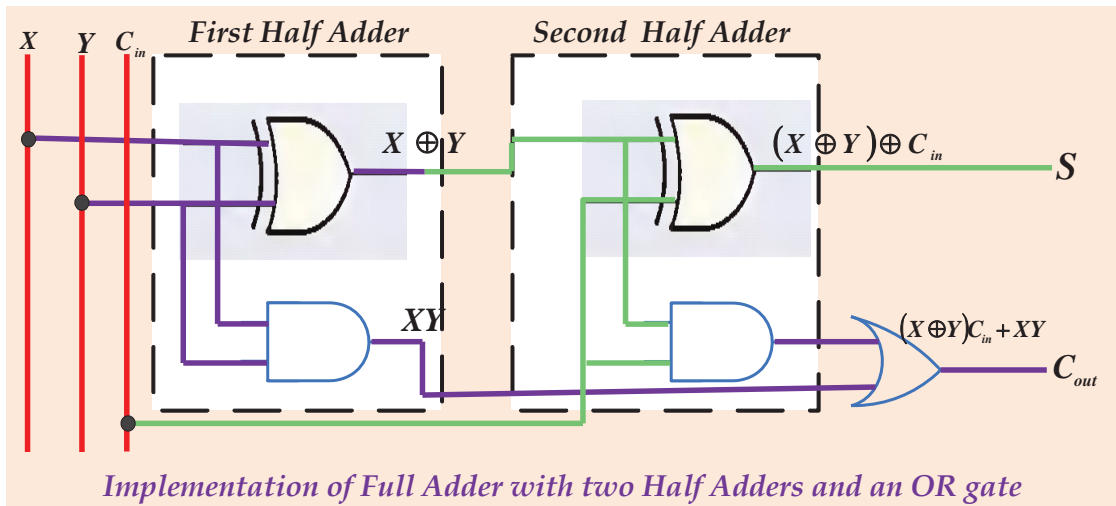
**The carry output:**

$$\begin{aligned} C_{out} &= \bar{X}Y C_{in} + X\bar{Y} C_{in} + XY C_{in} + XY \bar{C}_{in} \\ &= C_{in}(\bar{X}Y + X\bar{Y}) + XY(C_{in} + \bar{C}_{in}) \\ C_{out} &= C_{in} \cdot (X \oplus Y) + XY \end{aligned}$$


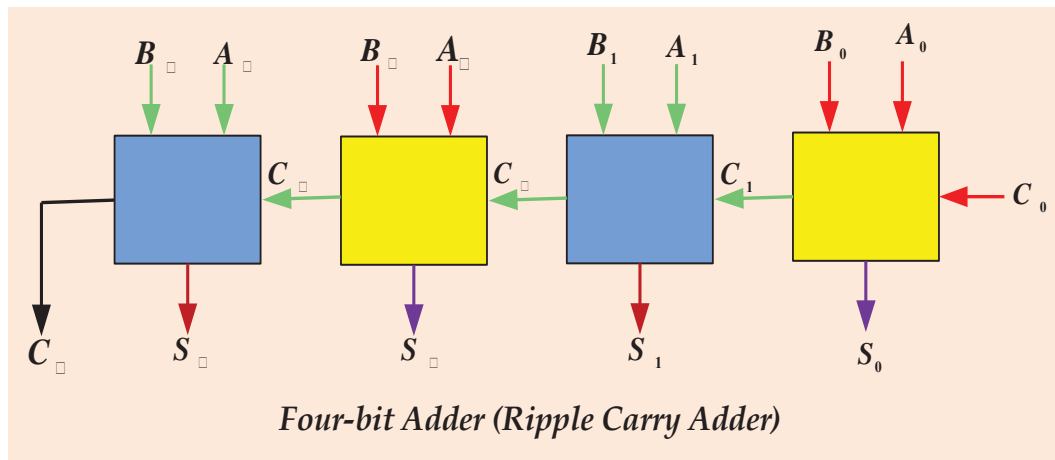
### 3. Binary Adder (Asynchronous Ripple-Carry Adder)

- A binary adder is a digital circuit that produces the *arithmetic sum of two binary numbers*.
- A binary adder can be constructed with *full adders connected in cascade* with the output carry from each full adder connected to the input carry of the next full adder in the chain.
- The *four-bit adder* is a typical example of a *standard component*. It can be used in many application involving arithmetic operations.



- The input carry to the adder is  $C_0$  and it ripples through the full adders to the output carry  $C_4$ .
- $n$ -bit binary adder requires  $n$  full adders.