

## 17.2 UJT (UNIUNCTION TRANSISTOR) RELAXATION OSCILLATOR

UJT is a three terminal semiconductor switching device. As it has only one PN junction and three leads, it is commonly called as Unijunction transistor.

The basic structure of UJT is shown in Fig. 17.1(a). It consists of a lightly doped N-type Silicon bar with a heavily doped P-type material alloyed to its one side closer to  $B_2$  for producing single PN junction. The circuit symbol of UJT is shown in Fig. 17.1(b). Here the emitter leg is drawn at an angle to the vertical and the arrow indicates the direction of the conventional current.

**Characteristics of UJT** Referring to Fig. 17.1(c), the interbase resistance between  $B_2$  and  $B_1$  of the silicon bar is  $R_{BB} = R_{B1} + R_{B2}$ . With emitter terminal open, if voltage  $V_{BB}$  is applied between the two bases, a voltage gradient is established along the N-type bar. The voltage drop across  $R_{B1}$  is given by  $V_1 = \eta V_{BB}$ , where the *intrinsic stand-off ratio*  $\eta = R_{B1}/(R_{B1} + R_{B2})$ . The typical value of  $\eta$  ranges from 0.56 to 0.75. This voltage  $V_1$  reverse biases the PN junction and emitter current is cut-off. But a small leakage current flows from  $B_2$  to emitter due to minority carriers. If a positive voltage  $V_E$  is applied to the emitter, the PN junction will remain reverse biased so long as  $V_E$  is less than  $V_1$ . If  $V_E$  exceeds  $V_1$  by the cutin voltage  $V_\gamma$ , the diode becomes forward biased. Under this condition, holes are injected into N-type bar. These holes are repelled by the terminal  $B_2$  and are attracted by the terminal  $B_1$ . Accumulation of holes in  $E$  to  $B_1$  region reduces the resistance in this section and hence emitter current  $I_E$  is increased and is limited by  $V_E$ . The device is now in the 'ON' state.

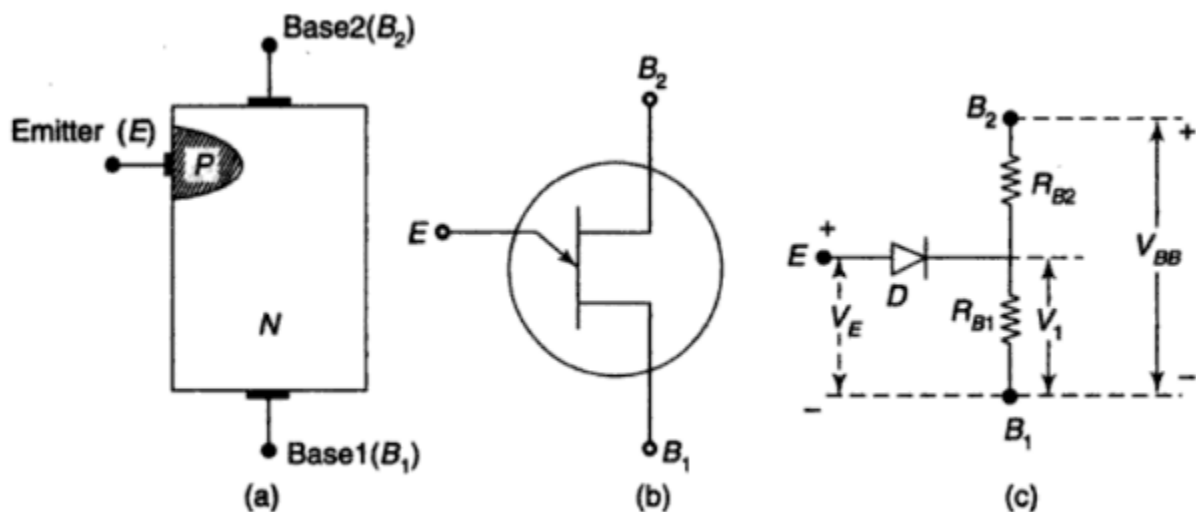


Fig. 17.1 UJT (a) Basic structure, (b) Circuit symbol, and (c) Equivalent circuit

If a negative voltage is applied to the emitter, PN junction remains reverse biased and the emitter current is cut off. The device is now in the 'OFF' state.

Figure 17.2 shows a family of input characteristics of UJT. Here, up to the peak point  $P$ , the diode is reverse biased and hence, the region to the left of the peak point is called *cut-off region*. The UJT has a stable firing voltage  $V_p$  which depends linearly on  $V_{BB}$  and a small firing current  $I_p$  ( $\approx 25 \mu\text{A}$ ). At  $P$ , the peak voltage  $V_p = \eta V_{BB} + V_\gamma$ , the diode starts conducting and holes are injected into N-layer. Hence, resistance decreases thereby decreasing  $V_E$  for the increase in  $I_E$ . So, there is a *negative resistance region* from peak point  $P$  to valley point  $V$ . After the valley point, the device is driven into saturation and behaves like a conventional forward biased PN junction diode. The region to the right of the valley point is called saturation region. In the valley point, the resistance changes from negative to positive. The resistance remains positive in the saturation region. For very large  $I_E$ , the characteristic asymptotically approaches the curve for  $I_{B2} = 0$ .


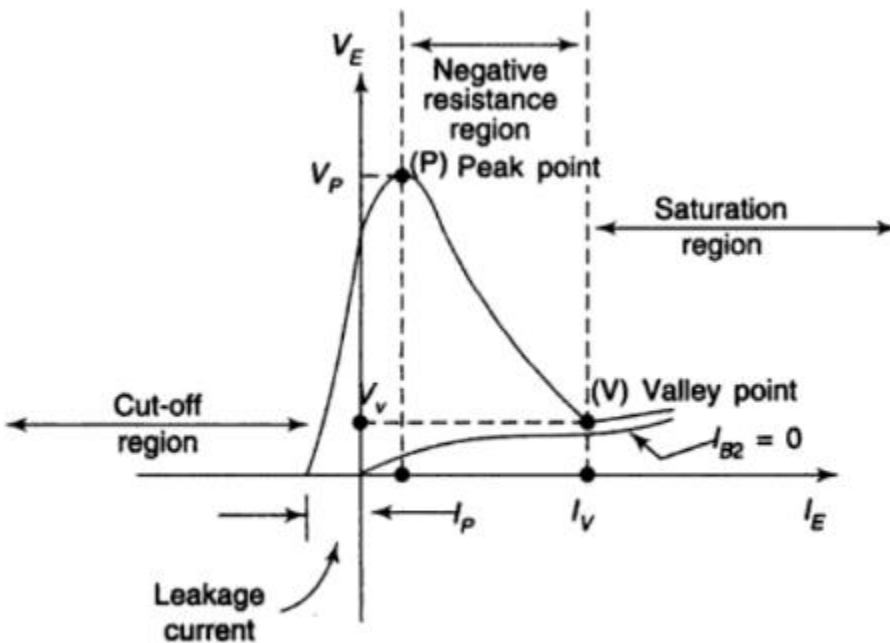


Fig. 17.2 Input characteristics of UJT

A unique characteristic of UJT is, when it is triggered, the emitter current increases regeneratively until it is limited by emitter power supply. Due to this negative resistance property, a UJT can be employed in a variety of applications, viz. sawtooth wave generator, pulse generator, switching, timing and phase control circuits.

**UJT relaxation oscillator** The relaxation oscillator using UJT which is meant for generating sawtooth waveform is shown in Fig. 17.3. It consists of a UJT and a capacitor  $C_E$  which is charged through  $R_E$  as the supply voltage  $V_{BB}$  is switched ON.

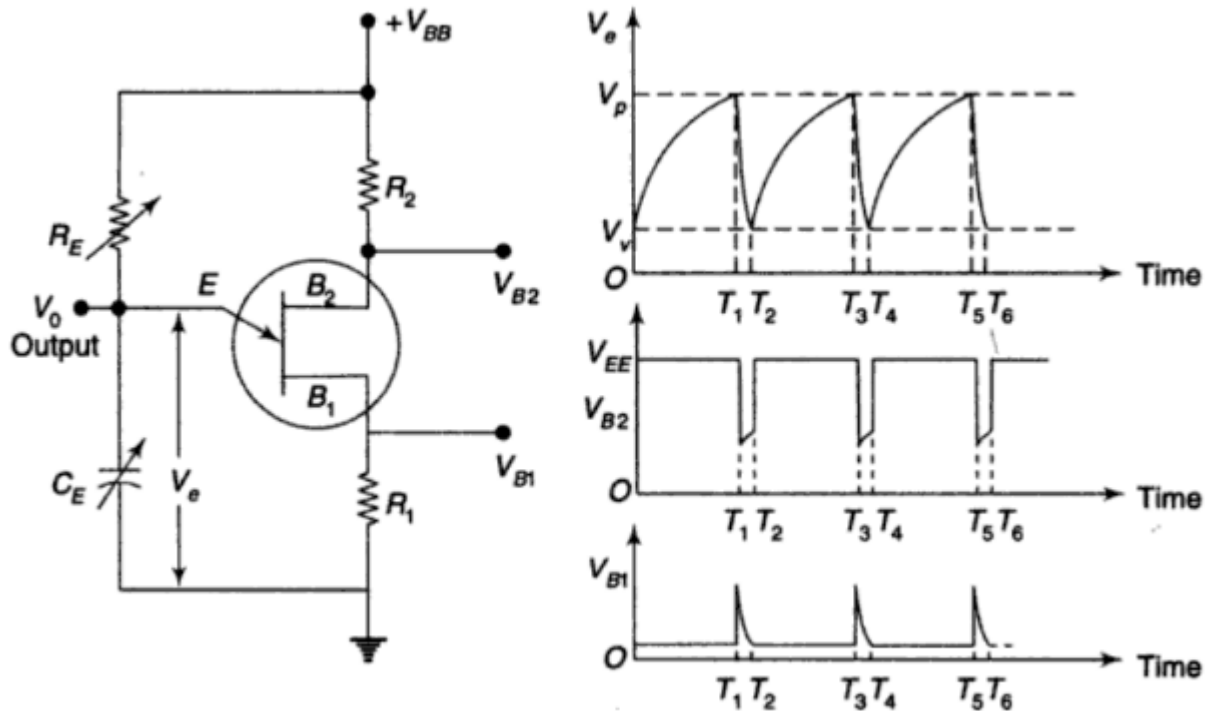

**Fig. 17.3** UJT Relaxation oscillator

The voltage across the capacitor increases exponentially and when the capacitor voltage reaches the peak point voltage  $V_p$ , the UJT starts conducting and the capacitor voltage is discharged rapidly through  $EB_1$  and  $R_1$ . After the peak point voltage of UJT is reached, it provides negative resistance to the discharge path which is useful in the working of the relaxation oscillator. As the capacitor voltage reaches zero, the device then cuts off and capacitor  $C_E$  starts to charge again. This cycle is repeated continuously generating a *sawtooth waveform* across  $C_E$ .

The inclusion of external resistors  $R_2$  and  $R_1$  in series with  $B_2$  and  $B_1$  provides spike waveforms. When the UJT fires, the sudden surge of current through  $B_1$  causes drop across  $R_1$ , which provides positive going spikes. Also, at the time of firing, fall of  $V_{EB1}$  causes  $I_2$  to increase rapidly which generates negative going spikes across  $R_2$ .

By changing the values of capacitance  $C_E$  or resistance  $R_E$ , frequency of the output waveform can be changed as desired, since these values control the time constant  $R_E C_E$  of the capacitor charging circuit.